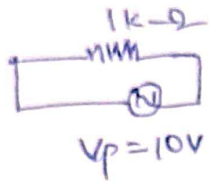


BEE Assignment-2

IT-A

A sinusoidal voltage is applied to the circuit as shown in figure



Determine RMS current, average current, peak current and peak to peak current.

Sol
$$\therefore V_{RMS} = \frac{V_P}{\sqrt{2}} \Rightarrow V_{RMS} = \frac{10}{\sqrt{2}} = \boxed{V_{RMS} = 7.071V}$$

$$I_{RMS} = \frac{V_{RMS}}{R} = \frac{7.071}{1000} = 7.071 \times 10^{-3}A$$

$$\Rightarrow \boxed{I_{RMS} = 7.071mA}$$

$$I_{avg} = I_0 \times 0.637$$

$$I_0 = I_{RMS} \times \sqrt{2} \Rightarrow \boxed{I_0 = 9.999mA}$$

$$I_{avg} = 9.999 \times 0.637$$

$$\boxed{I_{avg} = 6.369mA}$$


peak current, $I_P = ?$

$$I_P = \frac{V_P}{R} \Rightarrow I_P = \frac{10}{1000} \Rightarrow \boxed{I_P = 10mA}$$

peak to peak current

$$I_{P-P} = 2 \times 10mA = 20mA$$

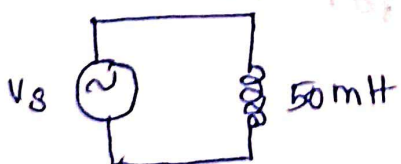2) Determine the RMS current in the circuit




$$V_{RMS} = 10V, f = 10kHz, L = 50mH$$

$$X_L = \omega L = 2\pi fL = 2\pi \times 10 \times 10^3 \times 50 \times 10^{-3}$$

$$\boxed{X_L = 3.14k\Omega}$$

$$I_{RMS} = \frac{V_{RMS}}{X_L} \Rightarrow I_{RMS} = \frac{10}{2.14 \times 10^{-3}} \Rightarrow \boxed{I_{RMS} = 3.18 \text{ mA}}$$

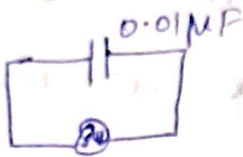3) determine the rms current in the circuit



$$V_{RMS} = 5 \text{ V}, f = 5 \text{ kHz}$$

$$C = 0.01 \mu\text{F}$$


$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C} = \frac{1}{2 \times 3.14 \times 5 \times 10^3 \times 0.01 \times 10^{-6}}$$

3) determine the rms current in the circuit

$$\boxed{X_C = 3.18 \text{ k}\Omega}$$

$$I_{RMS} = \frac{V_{RMS}}{X_C} = \frac{5}{3.18 \times 10^3} = 1.57 \text{ mA}$$

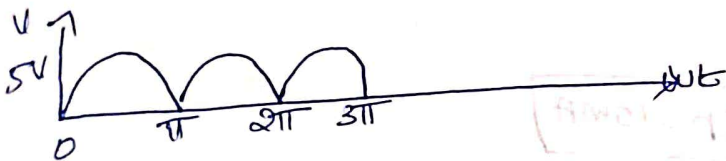
4) Find the average and rms values of wave rectified sine wave shown.



$$\text{Avg Value} = \frac{2 \times I_m}{\pi} = \frac{2 \times 5}{3.14} = \frac{10}{3.14} = 3.18$$

$$\text{rms Value} = \sqrt{\frac{25}{2}} = \sqrt{12.5} = 3.535$$

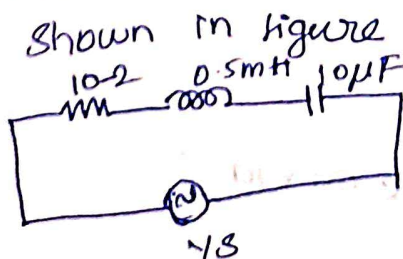5) determine the resonant frequency for the circuit shown in figure



Solu

$$f_r = \frac{1}{2\pi\sqrt{LC}} \Rightarrow f_n = \frac{1}{2 \times 3.14 \sqrt{0.3 \times 10^{-3} \times 10 \times 10^{-6}}}$$

$$= \frac{1}{2 \times 3.14 \times 2.23}$$

$$\boxed{f_r = 2.25 \text{ kHz}}$$

b) A voltage of $V(t) = 100 \sin \omega t$ is applied to a circuit. The current flowing through this circuit is $i(t) = 15 \sin(\omega t - 30^\circ)$

Sol

1) Determine the avg. power delivered to the circuit

$$\boxed{P_{avg} = VI \cos \phi}$$

$$\phi = 30^\circ, V_m = 100 \text{ V}, I_m = 15 \text{ A}$$

$$V_{rms} = \frac{V_m}{\sqrt{2}} = 70.71 \text{ V}$$

$$I_{rms} = \frac{I_m}{\sqrt{2}} = 10.60 \text{ A}$$

$$\Rightarrow P_{avg} = 70.71 \times 10.60 \times \cos(30^\circ)$$

$$\boxed{P_{avg} = 649.5 \text{ W}}$$


b) Apparent power, $S = VI = 70.71 \times 10.60$
 $= 749.526 \text{ VA}$

c) power factor ($\cos \phi$) = $\cos(30^\circ) = 0.866$

d) Reactive power, $Q = VI \sin \phi$
 $= 70.71 \times 10.60 \times \sin(30^\circ)$

$$Q = 374.763 \text{ VAR}$$

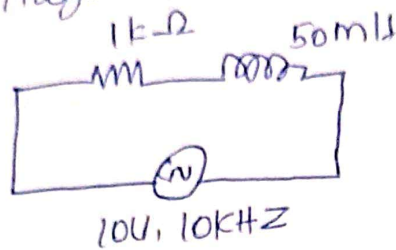7) RL: Find Impedance (Z), current (I), phase angle (ϕ), voltage across resistor V_R , voltage across inductor V_L .



i) $Z = \sqrt{R^2 + (X_L)^2}$

$$X_L = 2\pi f L = 2 \times 3.14 \times 10 \times 10^3 \times 50 \times 10^{-3} = 3.14 \Omega$$

$$\Rightarrow Z = \sqrt{(1000)^2 + (3.14)^2} = 3295.4 \text{ k}\Omega$$


(ii) $I = \frac{V}{Z} = \frac{10}{3.295.4 \times 10^3} = 3.03 \text{ mA}$

(iii) $\phi = \tan^{-1} \left(\frac{X_L}{R} \right) = \tan^{-1} \left(\frac{3.14}{1000} \right) = 72.33^\circ$

iv) $V_R = I \times R = 3.03 \times 10^{-3} \times 10^3 = 3.03 \text{ V}$

v) $V_L = I \times X_L = 3.03 \times 3.14 = 9.51 \text{ V}$

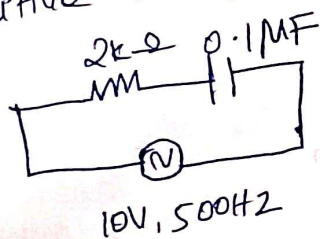8) RC: Determine total Impedance Z ; current I , phase angle ϕ , capacitive voltage V_C , resistive voltage V_R .



801:-

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C} = \frac{1}{2 \times 3.14 \times 500 \times 0.1 \times 10^{-6}} = 3180 \text{ k}\Omega$$

$$Z = \sqrt{R^2 + (X_C)^2} = \sqrt{2000^2 + 3180^2} = 3760.6 \text{ k}\Omega$$

$$I = \frac{V}{Z} = \frac{10}{3760.6} = 2.66 \text{ mA}$$


$$\phi = \tan^{-1} \left(\frac{X_C}{R} \right) = \tan^{-1} \left(\frac{-3180 \times 10^3}{2000} \right) = -57.87^\circ$$

ϕ ,
or V_L .

$$V_C = I(X_C) = 2.66 \times 10^{-3} \times 3180 \times 10^3 = 8.47 \text{ V}$$

$$V_R = I(R) = 2.66 \times 10^{-3} \times 2 \times 10^3 = 5.32 \text{ V}$$

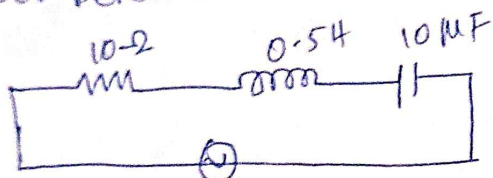9) RLC: determine the total Z , I , ϕ , V_R , V_L , V_C



50V, 50Hz

$$X_L = \omega L = 2\pi fL = 2 \times 3.14 \times 50 \times 0.5 = 157 \Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi fC} = \frac{1}{2 \times 3.14 \times 10 \times 10^{-6} \times 50} = 318.47 \Omega$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{(10)^2 + (157 - 318.47)^2}$$

$$\boxed{Z = 161.8 \Omega}$$

$$I = \frac{V}{Z} = \frac{50}{161.8} = 0.3 \text{ A}$$

angle ϕ ,

$$\phi = \tan^{-1} \left(\frac{X_L - X_C}{R} \right) = \tan^{-1} \left(\frac{157 - 318.47}{10} \right) = 318.47 \Omega$$

$$\boxed{Z = 161.8 \Omega}$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{(10)^2 + (157 - 318.47)^2}$$

$$I = \frac{V}{Z} = \frac{50}{161.8} = 0.3 \text{ A}$$

$$\phi = \tan^{-1} \left(\frac{X_L - X_C}{R} \right) = \tan^{-1} \left(\frac{157 - 318.47}{10} \right) = -86.45^\circ$$

$$V_L = I(X_L) = 0.3 \times 157 = 47.1 \text{ V}$$

$$V_R = I(R) = 0.3 \times 10 = 3 \text{ V}$$

$$V_C = I(X_C) = 0.3 \times 318.47 = 95.54 \text{ V}$$